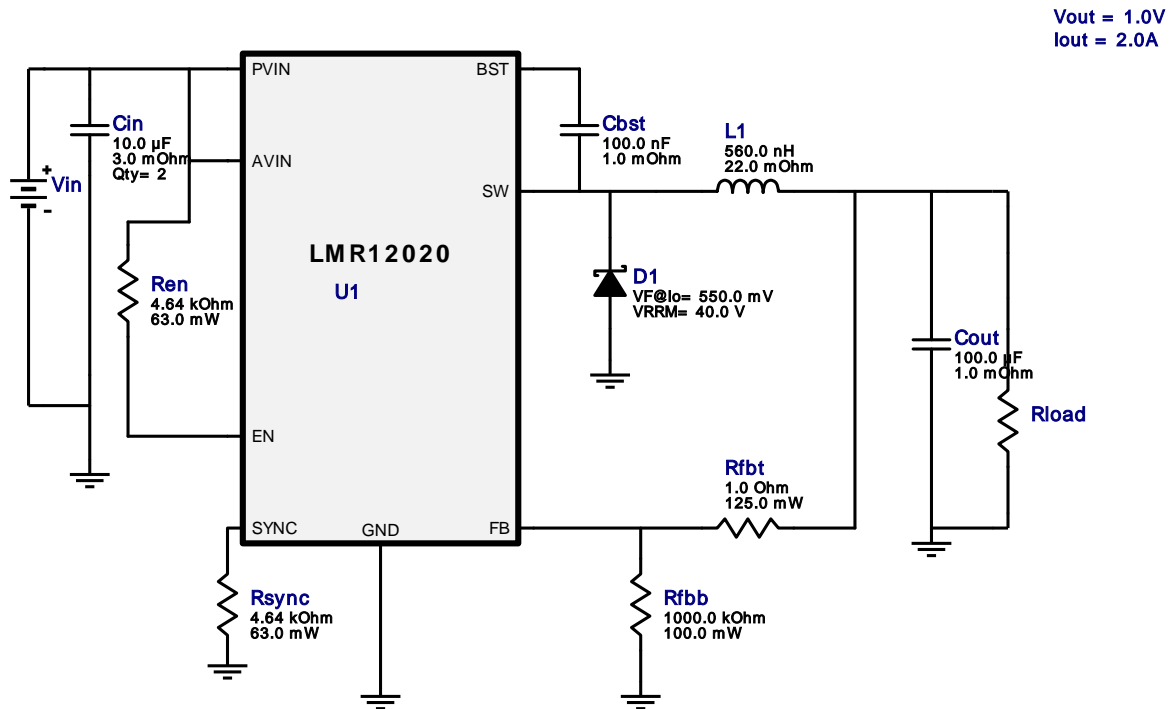


WEBENCH® Design Report

Design : 1 LMR12020XSD/NOPB
LMR12020XSD/NOPB 3.3V-3.3V to 1.00V @ 2A




VinMin = 3.3V
VinMax = 3.3V
Vout = 1.0V
Iout = 2.0A

Device = LMR12020XSD/NOPB
Topology = Buck
Created = 2023-02-08 04:31:42.665
BOM Cost = \$1.72
BOM Count = 11
Total Pd = 1.15W




Electrical BOM


Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
Cbst	Taiyo Yuden	EMK107B7104KA-T Series= X7R	Cap= 100.0 nF ESR= 1.0 mOhm VDC= 16.0 V IRMS= 0.0 A	1	\$0.01	0603 5 mm ²
Cin	Kemet	C0805C106K8PACTU Series= X5R	Cap= 10.0 uF ESR= 3.0 mOhm VDC= 10.0 V IRMS= 11.43 A	2	\$0.03	0805 7 mm ²
Cout	MuRata	GRM32EC80J107ME20L Series= X6S	Cap= 100.0 uF ESR= 1.0 mOhm VDC= 6.3 V IRMS= 6.0 A	1	\$0.17	1210_270 15 mm ²
D1	Fairchild Semiconductor	SS24FL	VF@Io= 550.0 mV VRRM= 40.0 V	1	\$0.09	SOD-123F 12 mm ²
L1	Vishay-Dale	IFSC1515AHERR56M01	L= 560.0 nH 22.0 mOhm	1	\$0.20	ELL6RH 67 mm ²
Ren	Vishay-Dale	CRCW04024K64FKED Series= CRCW..e3	Res= 4.64 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
Rfbb	Yageo	RC0603FR-071ML Series= ?	Res= 1000.0 kOhm Power= 100.0 mW Tolerance= 1.0%	1	\$0.01	0603 5 mm ²

Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
Rfbt	Vishay-Dale	CRCW08051R00FKEA Series= CRCW..e3	Res= 1.0 Ohm Power= 125.0 mW Tolerance= 1.0%	1	\$0.01	 0805 7 mm ²
Rsync	Vishay-Dale	CRCW04024K64FKED Series= CRCW..e3	Res= 4.64 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
U1	Texas Instruments	LMR12020XSD/NOPB	Switcher	1	\$1.15	 SDA10A 16 mm ²


IC Tj

 


Duty Cycle

 


Cin IRMS

 


PCB Layers






 








IC Ipk





 


L Pd

 

   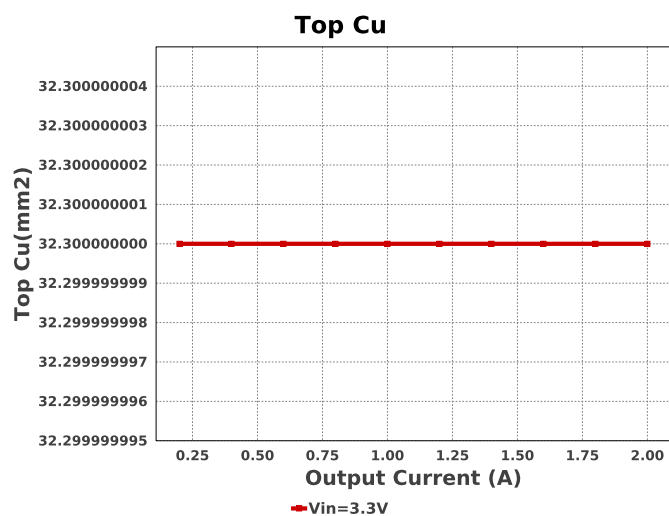  

      

     

Operating Values

#	Name	Value	Category	Description
1.	Bottom Cu	161.3 mm ²	Board_Layout	Recommended minimum area of bottom layer copper connected to DAP
2.	PCB Layers	2.0	Board_Layout	Recommended number of PCB layers for the necessary IC Thermal Resistance
3.	Thermal Vias	8.0	Board_Layout	Recommended number of 10 mil thermal vias under the IC
4.	Top Cu	32.3 mm ²	Board_Layout	Recommended minimum area of top layer copper connected to DAP
5.	Cin IRMS	988.594 mA	Capacitor	Input capacitor RMS ripple current
6.	Cin Pd	1.466 mW	Capacitor	Input capacitor power dissipation
7.	Cout IRMS	251.767 mA	Capacitor	Output capacitor RMS ripple current
8.	Cout Pd	63.387 μ W	Capacitor	Output capacitor power dissipation
9.	D1 Tj	67.97 degC	Diode	D1 junction temperature

#	Name	Value	Category	Description
10.	Diode Pd	632.83 mW	Diode	Diode power dissipation
11.	IC Ipk	0.0 A	IC	Peak switch current in IC
12.	IC Pd	416.22 mW	IC	IC power dissipation
13.	IC Tj	52.06 degC	IC	IC junction temperature
14.	IC Tolerance	16.0 mV	IC	IC Feedback Tolerance
15.	ICThetaJA	53.0 degC/W	IC	IC junction-to-ambient thermal resistance
16.	Iin Avg	953.75 mA	IC	Average input current
17.	L Ipp	872.15 mA	Inductor	Peak-to-peak inductor ripple current
18.	L Pd	96.8 mW	Inductor	Inductor power dissipation
19.	M Irms	1.303 A	Mosfet	MOSFET RMS ripple current
20.	M Vds Act	200.34 mV	Mosfet	Voltage drop across the MosFET
21.	Cin Pd	1.466 mW	Power	Input capacitor power dissipation
22.	Cout Pd	63.387 µW	Power	Output capacitor power dissipation
23.	Diode Pd	632.83 mW	Power	Diode power dissipation
24.	IC Pd	416.22 mW	Power	IC power dissipation
25.	L Pd	96.8 mW	Power	Inductor power dissipation
26.	Total Pd	1.147 W	Power	Total Power Dissipation
27.	BOM Count	11	System	Total Design BOM count
			Information	
28.	Duty Cycle	42.47 %	System	Duty cycle
			Information	
29.	Efficiency	63.545 %	System	Steady state efficiency
			Information	
30.	FootPrint	145.0 mm ²	System	Total Foot Print Area of BOM components
			Information	
31.	Frequency	2.0 MHz	System	Switching frequency
			Information	
32.	Iout	2.0 A	System	Iout operating point
			Information	
33.	Mode	CCM	System	Conduction Mode
			Information	
34.	Pout	2.0 W	System	Total output power
			Information	
35.	Total BOM	\$1.72	System	Total BOM Cost
			Information	
36.	Vin	3.3 V	System	Vin operating point
			Information	
37.	Vout	1.0 V	System	Operational Output Voltage
			Information	
38.	Vout Act	1.0 V	System	Achieved Vout with feedback resistor pair
			Information	
39.	Vout Actual	1.0 V	System	Vout Actual calculated based on selected voltage divider resistors
			Information	
40.	Vout Tolerance	1.6 %	System	Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable
			Information	
41.	Vout p-p	913.715 µV	System	Peak-to-peak output ripple voltage
			Information	

Design Inputs

Name	Value	Description
Iout	2.0	Maximum Output Current
VinMax	3.3	Maximum input voltage
VinMin	3.3	Minimum input voltage
Vout	1.0	Output Voltage
base_pn	LMR12020	Base Product Number
source	DC	Input Source Type
Ta	30.0	Ambient temperature

WEBENCH® Assembly

Component Testing

Some published data on components in datasheets such as Capacitor ESR and Inductor DC resistance is based on conservative values that will guarantee that the components always exceed the specification. For design purposes it is usually better to work with typical values. Since this data is not always available it is a good practice to measure the Capacitance and ESR values of C_{in} and C_{out} , and the inductance and DC resistance of $L1$ before assembly of the board. Any large discrepancies in values should be electrically simulated in WEBENCH to check for instabilities and thermally simulated in WebTHERM to make sure critical temperatures are not exceeded.

Soldering Component to Board

If board assembly is done in house it is best to tack down one terminal of a component on the board then solder the other terminal. For surface mount parts with large tabs, such as the DPAK, the tab on the back of the package should be pre-tinned with solder, then tacked into place by one of the pins. To solder the tab down to the board place the iron down on the board while resting against the tab, heating both surfaces simultaneously. Apply light pressure to the top of the plastic case until the solder flows around the part and the part is flush with the PCB. If the solder is not flowing around the board you may need a higher wattage iron (generally 25W to 30W is enough).

Initial Startup of Circuit

It is best to initially power up the board by setting the input supply voltage to the lowest operating input voltage 3.3V and set the input supply's current limit to zero. With the input supply off connect up the input supply to V_{in} and GND. Connect a digital volt meter and a load if needed to set the minimum load of the design from V_{out} and GND. Turn on the input supply and slowly turn up the current limit on the input supply. If the voltage starts to rise on the input supply continue increasing the input supply current limit while watching the output voltage. If the current increases on the input supply, but the voltage remains near zero, then there may be a short or a component misplaced on the board. Power down the board and visually inspect for solder bridges and recheck the diode and capacitor polarities. Once the power supply circuit is operational then more extensive testing may include full load testing, transient load and line tests to compare with simulation results.

Load Testing

The setup is the same as the initial startup, except that an additional digital voltmeter is connected between V_{in} and GND, a load is connected between V_{out} and GND and a current meter is connected in series between V_{out} and the load. The load must be able to handle at least rated output power + 50% (7.5 watts for this design). Ideally the load is supplied in the form of a variable load test unit. It can also be done in the form of suitably large power resistors. When using an oscilloscope to measure waveforms on the prototype board, the ground leads of the oscilloscope probes should be as short as possible and the area of the loop formed by the ground lead should be kept to a minimum. This will help reduce ground lead inductance and eliminate EMI noise that is not actually present in the circuit.



Design Assistance

1. Master key : 80AD6667D2B13DDF[v1]
2. **LMR12020** Product Folder : <http://www.ti.com/product/LMR12020> : contains the data sheet and other resources.

Important Notice and Disclaimer

TI provides technical and reliability data (including datasheets), design resources (including reference designs), application or other design advice, web tools, safety information, and other resources AS IS and with all faults, and disclaims all warranties. These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

Providing these resources does not expand or otherwise alter TI's applicable Terms of Sale or other applicable terms available either on ti.com or provided in conjunction with TI products.